

HW 3.3

Monday, February 10, 2020

10:49 PM

$$1: a) R = 10k\Omega \cdot e^{-4300 \left(\frac{1}{25} - \frac{1}{25} \right)}$$

$$R = 10k\Omega$$

$$\frac{10k\Omega}{20k\Omega} \cdot 3.3V = 1.65V$$

$$b) R = 10k\Omega \cdot e^{-4300 \left(\frac{1}{290.15} - \frac{1}{303.15} \right)} = 7860\Omega$$

$$\frac{10k\Omega}{10k\Omega + 7860\Omega} \cdot 3.3V = 1.85V$$

$$c) R = 10k\Omega \cdot e^{-4300 \left(\frac{1}{298.15} - \frac{1}{306.15} \right)} = 6860\Omega$$

$$\frac{10k\Omega}{10k\Omega + 6860\Omega} \cdot 3.3V = 1.96V$$

2: a)

$$\frac{1.65V}{3.3V} \cdot 4095 = 2048$$

$$b) \frac{1.85V}{3.3V} \cdot 4095 = 2296$$

$$c) \frac{1.96V}{3.3V} \cdot 4095 = 2432$$

3:

$$\frac{x}{3.3V} \cdot 4095 = \frac{2189 \cdot 3.3V}{4095} = 1.763V \text{ = minimum voltage}$$

$$\frac{2189 \cdot 3.3V}{4095} = 1.764V \text{ = maximum voltage}$$

4;

Temp for minimum voltage:

$$1.763V = 3.3V \cdot \frac{10k\Omega}{10k\Omega + R}$$

$$\downarrow$$

$$\frac{1.763V (10k\Omega + R)}{3.3V} = 10k\Omega$$

$$\downarrow$$

$$0.534 (10k\Omega + R) = 10k\Omega$$

$$\frac{0.534R}{0.534} = \frac{4.66k\Omega}{0.534}$$

$$\downarrow$$

$$R = 8.727k\Omega$$

$$R = 10k\Omega e^{-4300(1/298.15 - 1/T)}$$

$$\ln\left(\frac{8.727k\Omega}{10k\Omega}\right) = \frac{-4300(1/298.15 - 1/T)}{-4300}$$

$$-4300$$

$$\downarrow$$

$$3.167 \cdot 10^{-5} = \frac{1/298.15 - 1/T}{-1/298.15}$$

$$\underbrace{-0.00332} = -\frac{1}{T}$$

$$\downarrow$$

$$\frac{1}{0.00332} = T$$

$$\downarrow$$

$$300.992 \text{ Kelvin} = T$$

Temp for max voltage:

$$1.764V = 3.3V \cdot \frac{10k\Omega}{10k\Omega + R}$$

$$\downarrow$$
$$\frac{1.764V (10k\Omega + R)}{3.3V} = 10k\Omega$$

$$\downarrow$$
$$0.535 (10k\Omega + R) = 10k\Omega$$

$$\frac{0.535}{0.535} = \frac{4.65}{0.535}$$

$$\downarrow$$
$$R = 8.692 k\Omega$$

$$R = 10k\Omega e^{-4300 (1/298.15 - 1/T)}$$

$$\ln\left(\frac{8.692 k\Omega}{10k\Omega}\right) = \frac{-4300 (1/298.15 - 1/T)}{-4300}$$

$$-4300$$

$$\downarrow$$
$$3.260 \cdot 10^{-5} = \frac{1}{298.15} - \frac{1}{T}$$

$$- \frac{1}{298.15} \quad - \frac{1}{298.15}$$

$$\underbrace{\hspace{1cm}}_{-0.00332} = -\frac{1}{T}$$

$$\downarrow$$
$$\frac{1}{0.00332} = +$$

$$\downarrow$$
$$\textcircled{300.992 \text{ Kelvin} = +}$$

5. The resolution would go from 4096 to 1024 which is the equivalent to a resolution of $3/4$ from 4096.

6. The resolution would remain the same because the comparison of resistance and voltage is proportional with 3.3V to 5V and any other voltage.